 


Finite State Machines

General Sequential System




EC3057D MTDS - Winter 2020

Models of synchronous sequential systems

- Two common models of synchronous sequential systems
 - Moore machines
 - Mealy machines

EC3057D MTDS - Winter 2020


Moore Machine

 

Moore machine

EC3057D MTDS - Winter 2020


Mealy Machine

 

Mealy machine

EC3057D MTDS - Winter 2020

Design of a three-bit counter

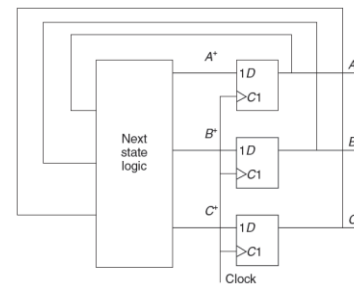


EC3057D MTDS - Winter 2020

ABC	$A^+B^+C^+$
000	001
001	010
010	011
011	100
100	101
101	110
110	111
111	000


EC3057D MTDS - Winter 2020

K-maps for 3-bit counter

 

EC3057D MTDS - Winter 2020

3-bit counter circuit

 


EC3057D MTDS - Winter 2020

Synchronous Sequential Circuit Analysis


Synchronous Sequential Circuit

 - **State Memory** – A set of n edge-triggered flip-flops that store the **current state** of the machine
 - All flip-flops are triggered from the same master clock signal
 - All flip-flops change state together
- **Combinational circuit**
 - Next state logic
 - Output logic – Mealy and Moore



EC3057D MTDS - Winter 2020

Mealy Model

 
Copyright © 2020 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

$$\text{next state} = F(\text{current state, inputs})$$

$$\text{outputs} = G(\text{current state, inputs})$$

EC3057D MTDS - Winter 2020

Moore Model

 

next state = $F(\text{current state, inputs})$

outputs = $G(\text{current state})$


EC3057D MTDIS - Winter 2020

Analysis - Goals

- Characterize as Mealy or Moore machine
- Determine next state equations, i.e., find the function F
 - next state = $F(\text{current state, inputs})$
- Determine output equations
 - Mealy: outputs = $G(\text{current state, inputs})$, or
 - Moore: outputs = $G(\text{current state})$
- Express as machine behavior
 - State table, or
 - State diagram
- Formulate English description of machine behavior

EC3057D MTDIS - Winter 2020


An example sequential circuit

 

- A sequential circuit with two JK flip-flops
- State or memory: Q_1Q_0
- One input: X ; One output: Z

EC3057D MTDIS - Winter 2020

State table of example circuit

 

Present State		Inputs X	Next State		Outputs Z
Q_1	Q_0		Q_1	Q_0	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

EC3057D MTDIS - Winter 2020

Output Equations

- From the diagram, you can see that

$$Z = Q_1Q_0X$$

Mealy model circuit !!!

Present State		Inputs X	Next State		Outputs Z
Q_1	Q_0		Q_1	Q_0	
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			0
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

EC3057D MTDIS - Winter 2020

Next State Equations – $Q(t+1)$


- Find the flip-flop input equations/excitation equations
- Substitute excitation equations in the flip-flop's characteristic equation

$$J_1 = X'Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

 

EC3057D MTDIS - Winter 2020

Next State Equations – Q(t+1)

- Excitation equations:

$$J_1 = X' Q_0 \text{ and } K_1 = X + Q_0$$

$$J_0 = X + Q_1 \text{ and } K_0 = X'$$

- Characteristic equation of the JK flip-flop:



EC3057D MTDS – Winter 2020

Next State Equations – Q(t+1)

- Excitation equations:


$$J_1 = X' Q_0 \text{ and } K_1 = X + Q_0$$

$$J_0 = X + Q_1 \text{ and } K_0 = X'$$

- Characteristic equation of the JK flip-flop:

$$Q(t+1) = K'Q(t) + JQ'(t)$$

- Next state equations:

 

EC3057D MTDS – Winter 2020

Next State Equations – Q(t+1)

- Excitation equations:

$$J_1 = X' Q_0 \text{ and } K_1 = X + Q_0$$

$$J_0 = X + Q_1 \text{ and } K_0 = X'$$

- Characteristic equation of the JK flip-flop:

$$Q(t+1) = K'Q(t) + JQ'(t)$$

- Next state equations:

$$\begin{aligned} Q_1(t+1) &= K_1'Q_1(t) + J_1Q_1'(t) \\ &= (X + Q_0(t))' Q_1(t) + X' Q_0(t) Q_1'(t) \\ &= X' (Q_0(t)' Q_1(t) + Q_0(t) Q_1'(t)) \\ &= X' (Q_0(t) \oplus Q_1(t)) \end{aligned}$$

$$\begin{aligned} Q_0(t+1) &= K_0'Q_0(t) + J_0Q_0'(t) \\ &= X Q_0(t) + (X + Q_1(t)) Q_0'(t) \\ &= X + Q_0(t)' Q_1(t) \end{aligned}$$

EC3057D MTDS – Winter 2020

State Table & Next State Equations

- $Q_1(t+1) = X' (Q_0(t) \oplus Q_1(t))$
 - $Q_1=0, Q_0=0, X=0 \Rightarrow Q_1(t+1)=0$
- $Q_0(t+1) = X + Q_0(t)' Q_1(t)$
 - $Q_1=0, Q_0=0, X=0 \Rightarrow Q_0(t+1)=0$

Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1

EC3057D MTDS – Winter 2020

State Table & Next State Equations

- $Q_1(t+1) = X' (Q_0(t) \oplus Q_1(t))$
 - $Q_1=0, Q_0=1, X=1 \Rightarrow Q_1(t+1)=0$
- $Q_0(t+1) = X + Q_0(t)' Q_1(t)$
 - $Q_1=0, Q_0=1, X=1 \Rightarrow Q_0(t+1)=1$

Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1

EC3057D MTDS – Winter 2020

State Table & Next State Equations

- $Q_1(t+1) = X' (Q_0(t) \oplus Q_1(t))$
- $Q_0(t+1) = X + Q_0(t)' Q_1(t)$

Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1

EC3057D MTDS – Winter 2020

State Table & Characteristic Table

- The general JK flip-flop characteristic equation is:

$$Q(t+1) = K'Q(t) + JQ'(t)$$
- We can also determine the next state for each input/current state combination directly from the characteristic table

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

EC3057D MTDS - Winter 2020

State Table & Characteristic Table

- With these equations, we can make a table showing J_1 , K_1 , J_0 and K_0 for the different combinations of present state Q_1Q_0 and input X

$$J_1 = X'Q_0 \quad J_0 = X + Q_1$$

$$K_1 = X + Q_0 \quad K_0 = X'$$

Present State		Inputs	Flip-flop Inputs			
Q_1	Q_0	X	J_1	K_1	J_0	K_0
0	0	0	0	0	0	1
0	0	1	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
1	0	0	0	0	1	1
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0

EC3057D MTDS - Winter 2020

State Table & Characteristic Table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Present State		Inputs	FF Inputs				Next State
Q_1	Q_0	X	J_1	K_1	J_0	K_0	Q_1 Q_0
0	0	0	0	0	0	1	
0	0	1	0	1	1	0	
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	
1	0	0	0	0	1	1	
1	0	1	0	1	1	0	
1	1	0	1	1	1	1	
1	1	1	0	1	1	0	

EC3057D MTDS - Winter 2020

State Table & Characteristic Table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Present State		Inputs	FF Inputs				Next State
Q_1	Q_0	X	J_1	K_1	J_0	K_0	Q_1 Q_0
0	0	0	0	0	0	1	
0	0	1	0	1	1	0	
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	
1	0	0	0	0	1	1	
1	0	1	0	1	1	0	
1	1	0	1	1	1	1	
1	1	1	0	1	1	0	

EC3057D MTDS - Winter 2020

A different look


Present State		Inputs	Next State		Outputs
Q_1	Q_0	X	Q_1	Q_0	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Present State Q1 Q0		Next State				Output Z	
		Input X= 0		Input X= 1		X= 0	X= 1
0	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	1

EC3057D MTDS - Winter 2020

State diagrams (Mealy model)

 
- We can also represent the state table graphically with a state diagram
- A diagram corresponding to our example state table is shown below



EC3057D MTDS - Winter 2020


Sizes of state diagrams

 - Always check the size of your state diagrams
 - If there are n flip-flops, there should be 2^n nodes in the diagram
 - If there are m inputs, then each node will have 2^m outgoing arrows
- In our example,
 - We have two flip-flops, and thus four states or nodes.
 - There is one input, so each node has two outgoing arrows.




EC3057D MTDS - Winter 2020

Another Mealy Circuit

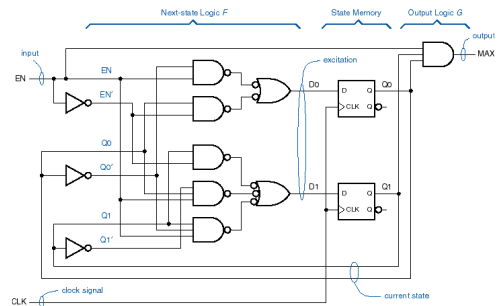Copyright © 2020 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

EC3057D MTDS - Winter 2020


Excitation Equations

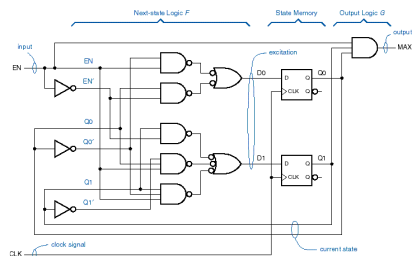Copyright © 2020 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

- $D_0 = EN' Q_0 + EN Q_0'$
- $D_1 = EN' Q_1 + EN Q_1' Q_0 + EN Q_1 Q_0'$

EC3057D MTDS - Winter 2020

Next State/Output Equations

 Copyright © 2020 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

- $Q_0(t+1) = D_0 = EN' Q_0 + EN Q_0'$
- $Q_1(t+1) = D_1 = EN' Q_1 + EN Q_1' Q_0 + EN Q_1 Q_0'$
- $MAX = EN Q_1 Q_0$

EC3057D MTDS - Winter 2020

Mealy State Table

- $Q_0(t+1) = D_0 = EN' Q_0 + EN Q_0'$
- $Q_1(t+1) = D_1 = EN' Q_1 + EN Q_1' Q_0 + EN Q_1 Q_0'$
- $MAX = EN Q_1 Q_0$

Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
0 0	0	0	0	0
0 1	0	1	0	0
1 0	1	0	1	0
1 1	1	0	0	1

EC3057D MTDS - Winter 2020

Mealy State Table


Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
0 0	0	0	0	0
0 1	0	1	0	0
1 0	1	0	1	0
1 1	1	0	0	1

Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
A	A	B	0	0
B	B	C	0	0
C	C	D	0	0
D	D	A	0	1

State Q1 Q0	State Name
0 0	A
0 1	B
1 0	C
1 1	D

EC3057D MTDS - Winter 2020


Mealy State Diagram

 

Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
A	A	B	0	0
B	B	C	0	0
C	C	D	0	0
D	D	A	0	1


EC3057D MTDS - Winter 2020

Moore Circuit

 Copyright © 2003 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

EC3057D MTDS - Winter 2020

Next State/Output Equations

 Copyright © 2003 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

- $Q_0(t+1) = D_0 = EN' Q_0 + EN Q_0'$
- $Q_1(t+1) = D_1 = EN' Q_1 + EN Q_1' Q_0 + EN Q_1 Q_0'$
- $MAX = Q_1 Q_0$

EC3057D MTDS - Winter 2020


Moore State Table

- $Q_0(t+1) = D_0 = EN' Q_0 + EN Q_0'$
- $Q_1(t+1) = D_1 = EN' Q_1 + EN Q_1' Q_0 + EN Q_1 Q_0'$
- $MAX = Q_1 Q_0$

Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
0 0	0 0	0 0	0	0
0 1	0 1	1 0	0	0
1 0	1 0	1 1	0	0
1 1	1 1	0 0	0	1

EC3057D MTDS - Winter 2020


Moore State Diagram

 

Present State Q1 Q0	Next State		Output MAX	
	Input EN= 0	Input EN= 1	EN= 0	EN= 1
0 0	0 0	0 1	0	0
0 1	0 1	1 0	0	0
1 0	1 0	1 1	0	0
1 1	1 1	0 0	0	1

EC3057D MTDS - Winter 2020

State Transitions

 Copyright © 2003 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3e

- MAX : Output of the Mealy circuit
- MAXS : Output of the Moore circuit

EC3057D MTDS - Winter 2020

Sequential circuit analysis summary

- To analyze sequential circuits, you have to:
 - Find Boolean expressions for the outputs of the circuit and the flip-flop inputs
 - Use these expressions to fill in the output and flip-flop input columns in the state table
 - Finally, use the characteristic equation or characteristic table of the flip-flop to fill in the next state columns.
- The result of sequential circuit analysis is a state table or a state diagram describing the circuit

EC3057D MITS - Winter 2020

Design of Sequence Detector

Sequence Detector

- A circuit that detects the occurrence of a particular pattern on its input is referred to as a sequence detector.


Design a circuit that examine a string of 0's and 1's applied to the input X and for any input sequence ending in 101 will produce an output Z=1 coincident with the last 1.

The circuit does not reset when a 1 output occur.

We assume that the input X can only change between clock pulses

EC3057D MITS - Winter 2020

101 Sequence Detector

 


X =	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0
Z =	0	0	0	0	0	1	0	0	0	0	1	0	1	0	0	0
(time:	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15)

EC3057D MITS - Winter 2020

Design of 101 Sequence Detector


- State Diagram:

 

EC3057D MITS - Winter 2020

Design of 101 Sequence Detector


- State Diagram:

 

EC3057D MITS - Winter 2020

Design of 101 Sequence Detector

- State Diagram (final):

 


EC3057D MTDS - Winter 2020

Design of 101 Sequence Detector

- State Table:

Present state	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
S_0	S_0	S_1	0	0
S_1	S_2	S_1	0	0
S_2	S_0	S_1	0	1

 

Assign a unique binary code to each state name (State Assignment)


- State Table with State Assignment:

AB	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1

EC3057D MTDS - Winter 2020


Design of Sequence Detector

- Derive Boolean Equations:

 


EC3057D MTDS - Winter 2020

Design of Sequence Detector

 

Compare with Typical Mealy Machine

 


EC3057D MTDS - Winter 2020

Design of Sequence Detector

- A Moore Sequence Detector:


101 sequence Detector

 

X = 0 0 1 1 0 1 1 0 0 1 0 1 0 1 0 0
 Z = 0 0 0 0 0 1 0 0 0 0 0 1 0 1 0 0
 (time: 0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15)


EC3057D MTDS - Winter 2020

Design of a Sequence Detector

 

EC3057D MTDS - Winter 2020

Design of a Sequence Detector

 

S_0 : start

S_1 : got 1

S_2 : got 10

S_3 : got 101

EC3057D MTDS – Winter 2020


Design of a Sequence Detector

S_0 : start

S_1 : got 1

S_2 : got 10

S_3 : got 101

 

EC3057D MTDS – Winter 2020

Design of a Sequence Detector

State Table

Present state	Next State		Present Output (Z)	AB	A ⁺ B ⁺		Z
	X = 0	X = 1			X = 0	X = 1	
S_0	S_0	S_1	0	00	00	01	0
S_1	S_2	S_1	0	01	11	01	0
S_2	S_0	S_3	0	11	00	10	0
S_3	S_2	S_1	1	10	11	01	1

Transition Table with State assignment

EC3057D MTDS – Winter 2020

State Diagram Development

- To develop a sequence detector state diagram:
 - Construct some sample input and output sequences to make sure that you understand the problem statement.
 - Begin in an initial state in which NONE of the initial portion of the sequence has occurred (typically “reset” state).
 - Add a state that recognizes that the first symbol has occurred.
 - Add states that recognize each successive symbol occurring.
 - Each time you add an arrow to the state graph, determine it can go to one of the previously defined states or whether a new state must be added.
 - The final state represents the input sequence occurrence.
 - Add state transition arcs which specify what happens when a symbol *not* in the proper sequence has occurred.
 - Check your state graph for completeness and non-redundant arcs.
 - When your state graph is complete, test it by applying the input sequences formulated in part I and making sure the output sequences are correct.

EC3057D MTDS – Winter 2020

Sequential circuit design procedure

Step 1:

Make a state table based on the problem statement. The table should show the present states, inputs, next states and outputs. (It may be easier to find a state diagram first, and then convert that to a table)

Step 2:

Assign binary codes to the states in the state table, if you haven't already. If you have n states, your binary codes will have at least $\lceil \log_2 n \rceil$ digits, and your circuit will have at least $\lceil \log_2 n \rceil$ flip-flops

Step 3:

For each flip-flop and each row of your state table, find the flip-flop input values that are needed to generate the next state from the present state. You can use flip-flop excitation tables here.

Step 4:

Find simplified equations for the flip-flop inputs and the outputs.

Step 5:

Build the circuit!

EC3057D MTDS – Winter 2020

Another Example

Sequence detector (Mealy)

- A **sequence detector** is a special kind of sequential circuit that looks for a special bit pattern in some input
- The detector circuit has only one input, X
 - One bit of input is supplied on every clock cycle
 - This is an easy way to permit arbitrarily long input sequences
- There is one output, Z, which is 1 when the desired pattern is found
- Our example will detect the bit pattern "1001":

Inputs: 1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...
 Outputs: 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 0 ...
- A sequential circuit is required because the circuit has to "remember" the inputs from previous clock cycles, in order to determine whether or not a match was found

EC3057D MTDS - Winter 2020


Step 1: Making a state table

- The first thing you have to figure out is precisely how the use of state will help you solve the given problem
 - Make a state table based on the problem statement. The table should show the present states, inputs, next states and outputs
 - Sometimes it is easier to first find a state diagram and then convert that to a table
- This is usually the most difficult step. Once you have the state table, the rest of the design procedure is the same for all sequential circuits

EC3057D MTDS - Winter 2020

A basic Mealy state diagram

 
- What state do we need for the sequence detector?
 - We have to "remember" inputs from previous clock cycles
 - For example, if the previous three inputs were 100 and the current input is 1, then the output should be 1
 - In general, we will have to remember occurrences of parts of the desired pattern—in this case, 1, 10, and 100
- We'll start with a basic state diagram:



EC3057D MTDS - Winter 2020

Overlapping occurrences of the pattern

 
- What happens if we're in state D (the last three inputs were 100), and the current input is 1?
 - The output should be a 1, because we've found the desired pattern
 - But this last 1 could also be the start of another occurrence of the pattern! For example, 1001001 contains *two* occurrences of 1001
 - To detect overlapping occurrences of the pattern, the next state should be B.



EC3057D MTDS - Winter 2020


Filling in the other arrows

 - Two* outgoing arrows for each node, to account for the possibilities of X=0 and X=1
- The remaining arrows we need are shown in blue. They also allow for the correct detection of overlapping occurrences of 1001.



EC3057D MTDS - Winter 2020

Mealy state diagram & table

 

EC3057D MTDS - Winter 2020

Step 2: Assigning binary codes to states

- We have four states ABCD, so we need at least two flip-flops Q_1Q_0
- The easiest thing to do is represent state A with $Q_1Q_0 = 00$, B with 01, C with 10, and D with 11
- The state assignment can have a big impact on circuit complexity, but we won't worry about that too much in this class

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

Present State		Input X	Next State		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

EC3057D MTDS - Winter 2020

Step 3: Finding flip-flop input values

- Next we have to figure out how to actually make the flip-flops change from their present state into the desired next state
- This depends on what kind of flip-flops you use!
- We'll use two JKs. For each flip-flop Q_i , look at its present and next states, and determine what the inputs J_i and K_i should be in order to make that state change.

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0					0
0	0	1	0	1					0
0	1	0	1	0					0
0	1	1	0	1					0
1	0	0	1	1					0
1	0	1	0	1					0
1	1	0	0	0					0
1	1	1	0	1					1

EC3057D MTDS - Winter 2020

JK excitation table

- An **excitation table** shows what flip-flop inputs are required in order to make a desired state change

$Q(t)$	$Q(t+1)$	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set

- This is the same information that's given in the characteristic table, but presented "backwards"

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

EC3057D MTDS - Winter 2020

- Use the JK excitation table on the right to find the correct values for *each* flip-flop's inputs, based on its present and next states

$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Present State		Input	Next State		Flip flop inputs				Output
Q_1	Q_0	X	Q_1	Q_0	J_1	K_1	J_0	K_0	Z
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	x	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

EC3057D MTDS - Winter 2020

Step 4: Find equations for the FF inputs and output

- Now you can make K-maps and find equations for each of the four flip-flop inputs, as well as for the output Z.
- These equations are in terms of the present state and the inputs
- The advantage of using JK flip-flops is that there are many don't care conditions, which can result in simpler MSP equations

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

EC3057D MTDS - Winter 2020

FF input equations

Present State		Input	Next State		Flip flop inputs					Output
Q_1	Q_0		Q_1	Q_0	J_1	K_1	J_0	K_0	Z	
0	0	0	0	0	0	x	0	x	0	
0	0	1	0	1	0	x	1	x	0	
0	1	0	1	0	1	x	x	1	0	
0	1	1	0	1	0	x	x	0	0	
1	0	0	1	1	x	0	1	x	0	
1	0	1	0	1	x	1	1	x	0	
1	1	0	0	0	x	1	x	1	0	
1	1	1	0	1	x	1	x	0	1	

J_1	Q_1	Q_0	
00	01	11	10
0	0	1	x
1	0	0	x

$$J_1 = X'Q_0$$

K_1	Q_1	Q_0	
00	01	11	10
0	x	x	1
1	x	x	1

$$K_1 = X + Q_0$$

EC3057D MTDS - Winter 2020

FF input equations

Present State	Input	Next State	Flip flop inputs	Output
$Q_1 Q_0$	X	$Q_1 Q_0$	$J_1 K_1 J_0 K_0$	Z
0 0	0	0 0	0 x 0 x	0
0 0	1	0 1	0 x 1 x	0
0 1	0	1 0	1 x x 1	0
0 1	1	0 1	0 x x 0	0
1 0	0	1 1	x 0 1 x	0
1 0	1	0 1	x 1 1 x	0
1 1	0	0 0	x 1 x 1	0
1 1	1	0 1	x 1 x 0	1

J_0	$Q_1 Q_0$
00	01
01	11
10	01
11	11

K_0	$Q_1 Q_0$
00	01
01	11
10	01
11	11

$$J_0 = X + Q_1$$

$$K_0 = X'$$

EC3057D MTDS - Winter 2020

Output equation

Present State	Input	Next State	Flip flop inputs	Output
$Q_1 Q_0$	X	$Q_1 Q_0$	$J_1 K_1 J_0 K_0$	Z
0 0	0	0 0	0 x 0 x	0
0 0	1	0 1	0 x 1 x	0
0 1	0	1 0	1 x x 1	0
0 1	1	0 1	0 x x 0	0
1 0	0	1 1	x 0 1 x	0
1 0	1	0 1	x 1 1 x	0
1 1	0	0 0	x 1 x 1	0
1 1	1	0 1	x 1 x 0	1


Z	$Q_1 Q_0$
00	01
01	11
10	01
11	11

$$Z = X Q_1 Q_0$$

EC3057D MTDS - Winter 2020

Step 5: Build the circuit

 - Lastly, we use these simplified equations to build the completed circuit



EC3057D MTDS - Winter 2020

Sequence detector (Moore)


- A **sequence detector** is a special kind of sequential circuit that looks for a special bit pattern in some input
- The detector circuit has only one input, X
 - One bit of input is supplied on every clock cycle
 - This is an easy way to permit arbitrarily long input sequences
- There is one output, Z , which is 1 when the desired pattern is found
- Our example will detect the bit pattern "1001":

Inputs: 1 1 1 0 0 1 1 0 1 0 0 0 1 0 0 1 1 0 ...
 Outputs: 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 0 ...

- A sequential circuit is required because the circuit has to "remember" the inputs from previous clock cycles, in order to determine whether or not a match was found

EC3057D MTDS - Winter 2020

Moore state diagram & table

 

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	E	1
E	0	C	1
E	1	B	1

Circuit design is left as an exercise !

EC3057D MTDS - Winter 2020

Comparison of Mealy and Moore FSM

- Mealy machines have less states**
 - outputs are on transitions (n^2) rather than states (n)
- Moore machines are safer** to use
 - outputs change at clock edge (always one cycle later)
 - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback **may** occur if one isn't careful
- Mealy machines react faster** to inputs
 - react in same cycle – don't need to wait for clock
 - outputs **may** be considerably shorter than the clock cycle
 - in Moore machines, more logic **may** be necessary to decode state into outputs – there **may** be more gate delays after clock edge


EC3057D MTDS - Winter 2020

Example: Sequence Detector

A sequential circuit has one input (X) and one output (Z). The circuit examines groups of four consecutive inputs and produces an output $Z = 1$ if the input sequence 0101 or 1001 occurs. The circuit resets after every four inputs. Find a Mealy state graph. A typical input and output sequence is:


$X = 0101$	0010	1001	0100
$Z = 0001$	0000	0001	0000

EC3057D MTDS - Winter 2020

 


EC3057D MTDS - Winter 2020

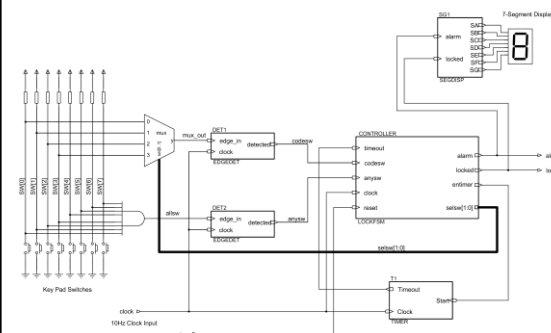Combination Lock FSM with Automatic Lock Feature



EC3057D MTDS - Winter 2020

Logic diagram of edge detector edgedet

 

```

1 module edgedet(input edge_in,
2                 output detected,
3                 input clock);
4
5 wire q0, q1;
6
7 dff dff0(.q(q0), .d(edge_in), .clk(clock));
8 dff dff1(.q(q1), .d(q0), .clk(clock));
9
10 assign detected = q0 & ~q1;
11
12 endmodule

```

EC3057D MTDS - Winter 2020

Timer

```

1 module Timer(input Clock, Start, output Timeout);
2 //time delay value in clk pulses
3 localparam NUMCLKS = 300;
4
5 reg [8:0] q;
6 always @(posedge Clock)
7 begin
8   if (!Start || (q == NUMCLKS))
9     q <= 9'b0;
10  else
11    q <= q + 1;
12 end
13 //decode counter output
14 assign Timeout = (q == NUMCLKS);
15
16 endmodule

```

EC3057D MTDS - Winter 2020

Seven Segment Display


```

1 module segdisp(input locked, alarm,
2                output SA, SB, SC, SD, SE, SF, SG);
3
4 reg [6:0] seg;
5
6 always @(locked or alarm)
7 begin
8   if (alarm == 0)
9     seg = 7'b0001000; //display 'A'
10  else if (locked == 0)
11    seg = 7'b1000001; //display 'U'
12  else
13    seg = 7'b1110001; //display 'L'
14 end
15
16 assign (SA, SB, SC, SD, SE, SF, SG) = seg;
17
18 endmodule

```

EC3057D MTDS - Winter 2020

FSM

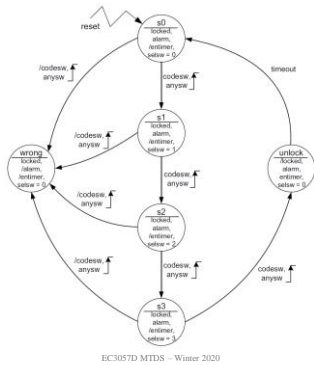

EC3057D MTDS - Winter 2020

```

1  module lockfsm(input clock, reset,
2      codesw, anysw,
3      output reg [1:0] selsw,
4      output locked, alarm, entimer,
5      input timeout);
6  localparam s0=3'b000, s1=3'b001, s2=3'b010,
7      s3=3'b011,
8      wrong=3'b100, unlock=3'b101;
9  reg [2:0] lockstate;
10 always @(posedge clock or posedge reset)
11 begin
12 if (reset == 1'b1)
13 lockstate <= s0;
14 else
15 case (lockstate)
16 s0 : if (anysw & codesw)
17 lockstate <= s1;
18 else if (anysw)
19 lockstate <= wrong;
20 else
21 lockstate <= s0;
22 s1 : if (anysw & codesw)
23 lockstate <= s2;
24 else if (anysw)
25 lockstate <= wrong;
26 else
27 lockstate <= s1;
28 s2 : if (anysw & codesw)
29 lockstate <= s3;
30 else if (anysw)
31 lockstate <= wrong;

```

EC3057D MTDS - Winter 2020

```

32 else
33 lockstate <= s2;
34 s3: if (anysw & codesw)
35 lockstate <= unlock;
36 else if (anysw)
37 lockstate <= wrong;
38 else
39 lockstate <= s3;
40 wrong: lockstate <= wrong;
41 unlock: if (timeout)
42 lockstate <= s0;
43 else
44 lockstate <= unlock;
45 default: lockstate <= 3'bx;
46 endcase
47 end

```

EC3057D MTDS - Winter 2020

```

48 always @(lockstate)
49 begin
50 case (lockstate)
51 s0: selsw = 0;
52 s1: selsw = 1;
53 s2: selsw = 2;
54 s3: selsw = 3;
55 wrong: selsw = 0;
56 unlock: selsw = 0;
57 default: selsw = 2'bx;
58 endcase
59 end
60 assign locked = (lockstate == unlock) ? 0 : 1;
61 assign alarm = (lockstate == wrong) ? 0 : 1;
62 assign entimer = (lockstate == unlock) ? 1 : 0;
63 endmodule

```

EC3057D MTDS - Winter 2020

```

1  module comblock(input clock, clear,
2      input [7:0] switches,
3      output alarm, locked,
4      output SA, SB, SC, SD, SE, SF, SG);
5  wire mux_out, anysw, codesw,
6      allow, entimer, timeout;
7  wire [1:0] selsw;
8  //4-to-1 multiplexor
9  assign mux_out = selsw == 0 ? switches[0] :
10 (selsw == 1 ? switches[1] :
11 (selsw == 2 ? switches[2] :
12 (selsw == 3 ? switches[3] : 1'b0)));
13 //AND gate for all switches
14 assign allow = &switches;
15 edgeset det1(.edge_in(mux_out),
16 .detected(codesw),
17 .clock(clock));
18 edgeset det2(.edge_in(allow),
19 .detected(anysw),
20 .clock(clock));
21 Timer tl(.Clock(clock),
22 .Start(entimer),
23 .Timeout(timeout));
24 lockfsm controller(.clock(clock),
25 .reset(clear),
26 .codesw(codesw),
27 .anysw(anysw),
28 .selsw(selsw),
29 .locked(locked),
30 .alarm(alarm),
31 .entimer(entimer),
32 .timeout(timeout));

```

EC3057D MTDS - Winter 2020

```

33 segdisp sgl (.locked(locked),
34 .alarm(alarm),
35 .SA(SA),
36 .SB(SB),
37 .SC(SC),
38 .SD(SD),
39 .SE(SE),
40 .SF(SF),
41 .SG(SG));
42 endmodule

```

EC3057D MTDS - Winter 2020

