 


Synthesis of Digital Circuits

Logic Synthesis

- Verilog and VHDL started out as simulation languages, but soon programs were written to automatically convert Verilog code into low-level circuit descriptions (netlists).



- Synthesis* converts Verilog (or other HDL) descriptions to an implementation using technology-specific primitives:
 - For FPGAs: LUTs, flip-flops, and RAM blocks
 - For ASICs: standard cell gate and flip-flop libraries, and memory blocks

EC3057D MTDs - Winter 2020

2

Why Perform Logic Synthesis?

- Automatically manages many details of the design process:
 - Fewer bugs
 - Improves productivity
- Abstracts the design data (HDL description) from any particular implementation technology
 - Designs can be re-synthesized targeting different chip technologies; E.g.: first implement in FPGA then later in ASIC
- In some cases, leads to a more optimal design than could be achieved by manual means (e.g.: logic optimization)

Why Not Logic Synthesis?

- May lead to less than optimal designs in some cases

EC3057D MTDs - Winter 2020

3

How Does It Work?


- Variety of general and ad-hoc (special case) methods:
 - Instantiation:** maintains a library of primitive modules (AND, OR, etc.) and user defined modules
 - "Macro expansion"/substitution:** a large set of language operators (+, -, Boolean operators, etc.) and constructs (if-else, case) expand into special circuits
 - Inference:** special patterns are detected in the language description and treated specially (e.g.: inferring memory blocks from variable declaration and read/write statements, FSM detection and generation from "always @ (posedge clk)" blocks)
 - Logic optimization:** Boolean operations are grouped and optimized with logic minimization techniques
 - Structural reorganization:** advanced techniques including sharing of operators, and retiming of circuits (moving FFs), and others

EC3057D MTDs - Winter 2020

4

Operators

- Logical operators map into primitive logic gates
- Arithmetic operators map into adders, subtractors, ...
 - Unsigned 2s complement
 - Model carry: target is one-bit wider than source
 - Watch out for *, %, and /
- Relational operators generate comparators
- Shifts by constant amount are just wire connections
 - No logic involved
- Variable shift amounts a whole different story --- shifter
- Conditional expression generates logic or MUX

 


EC3057D MTDs - Winter 2020

5

Synthesis vs. Compilation

Levels of Representation

 

```

temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
  
```

```

lw $t0, 0($2)
lw $t1, 4($2)
sw $t1, 0($2)
sw $t0, 4($2)
  
```

```

0000 1001 1100 0110 1010 1111 01
1010 1111 0101 1000 0000 1001 11
1100 0110 1010 1111 0101 1000 00
0101 1000 0000 1001 1100 0110 10
  
```

- Compiler**
 - Recognizes all possible constructs in a formally defined program language
 - Translates them to a machine language representation of execution process
- Synthesis**
 - Recognizes a target dependent subset of a hardware description language
 - Maps to collection of concrete hardware resources
 - Iterative tool in the design flow


EC3057D MTDs - Winter 2020

6

Simple Example

```
module foo (a,b,s0,s1,f);
input [3:0] a;
input [3:0] b;
input s0,s1;
output [3:0] f;
reg f;
always @ (a or b or s0 or s1)
if (!s0 && s1 || s0) f=a; else f=b;
endmodule
```

 - Should expand if-else into 4-bit wide multiplexer (a, b, f are 4-bit vectors) and optimize/minimize the control logic:



EC3057D MTDS - Winter 2020

7

Module Template

Synthesis tools expects to find modules in this format.

```
module <top_module_name>(<port list>);
/* Port declarations. followed by wire, reg, integer, task and function
declarations */
/* Describe hardware with one or more continuous assignments, always blocks, module instantiations and
gate instantiations */
// Continuous assignment
wire <result_signal_name>;
assign <result_signal_name> = <expression>;
// always block
always @(<event_expression>)
begin
// Procedural assignments
// if statements
// case, casex, and casez statements
// while, repeat and for loops
// user task and user function calls
end
// Module instantiation
<module_name> <instance_name> (<port list>);
// Instantiation of built-in gate primitive
gate_type_keyword (<port list>);
endmodule
```

- Order of these statements is irrelevant, all execute concurrently
- Statements between the **begin** and **end** in an always block execute sequentially from top to bottom (however, beware of blocking versus non-blocking assignment)
- Statements within a fork-join statement in an always block execute concurrently

EC3057D MTDS - Winter 2020

8

Procedural Assignments

- Verilog has two types of assignments within always blocks:
- Blocking** procedural assignment "="
 - RHS is executed and assignment is completed before the next statement is executed; e.g., Assume A holds the value 1 ... A<=2; B=A; A is left with 2, B with 2.
- Non-blocking** procedural assignment "<="
 - RHS is executed and assignment takes place at the end of the current time step (not clock cycle); e.g., Assume A holds the value 1 ... A<=2; B<=A; A is left with 2, B with 1.
- Notion of "current time step" is tricky in synthesis, so to guarantee that your simulation matches the behavior of the synthesized circuit, follow these rules:
 - Use blocking assignments to model combinational logic within an always block
 - Use non-blocking assignments to implement sequential logic
 - Do not mix blocking and non-blocking assignments in the same always block
 - Do not make assignments to the same variable from more than one always block

EC3057D MTDS - Winter 2020

9

Combinational Logic

CL can be generated using:

- Primitive gate instantiation: **AND**, **OR**, etc.
- Continuous assignment (assign keyword), example:

```
Module adder_8 (cout, sum, a, b, cin);
output cout;
output [7:0] sum;
input cin;
input [7:0] a, b;
assign {cout, sum} = a + b + cin;
endmodule
```
- Always block:

```
always @ (event_expression)
begin
// procedural assignment statements, if statements,
// case statements, while, repeat, and for loops.
// Task and function calls
end
```

EC3057D MTDS - Winter 2020

10

VERILOG: Synthesis - Combinational Logic

- Combination logic function can be expressed as:

logic_output(t) = f(logic_inputs(t))



Rules

- Avoid technology dependent modeling; i.e. implement functionality, not timing.
- The combinational logic must not have feedback.
- Specify the output of a combinational behavior for all possible cases of its inputs.
- Logic that is not combinational will be synthesized as sequential.

EC3057D MTDS - Winter 2020

11

Styles for Synthesizable Combinational Logic

- Synthesizable combinational can have following styles
 - Netlist of gate instances and Verilog primitives (Fully structural)
 - Combinational UDP (Some tools)
 - Functions
 - Continuous Assignments
 - Behavioral statements
 - Tasks without event or delay control
 - Interconnected modules of the above


EC3057D MTDS - Winter 2020

12

Synthesis of Combinational Logic – Gate Netlist

- Synthesis tools further optimize a gate netlist specified in terms of Verilog primitives
- Example:
 
```
module or_nand_1 (enable, x1, x2, x3, x4, y);
  input enable, x1, x2, x3, x4;
  output y;
  wire w1, w2, w3;
  or (w1, x1, x2);
  or (w2, x3, x4);
  or (w3, x3, x4); // redundant
  nand (y, w1, w2, w3, enable);
endmodule
```



EC3057D MTDS - Winter 2020

13

Synthesis of Combinational Logic – Gate Netlist (cont.)

- General Steps:
 - Logic gates are translated to Boolean equations.
 - The Boolean equations are optimized.
 - Optimized Boolean equations are covered by library gates.
 - Complex behavior that is modeled by gates is not mapped to complex library cells (e.g. adder, multiplier)
 - The user interface allows gate-level models to be preserved in synthesis.


EC3057D MTDS - Winter 2020

14

Synthesis of Combinational Logic – Continuous Assignments

Example:

```
module or_nand_2 (enable, x1, x2, x3, x4, y);
  input enable, x1, x2, x3, x4;
  output y;
  assign y = !(enable & (x1 | x2) & (x3 | x4));
endmodule
```

 

EC3057D MTDS - Winter 2020

15

Synthesis of Combinational Logic – Behavioral Style

Example:

```
module or_nand_3 (enable, x1, x2, x3, x4, y);
  input enable, x1, x2, x3, x4;
  output y;
  reg y;
  always @ (enable or x1 or x2 or x3 or x4)
    if (enable)
      y = !(x1 | x2) & (x3 | x4);
    else
      y = 1; // operand is a constant.
endmodule
```

Note: Inputs to the behavior must be included in the event control expression, otherwise a latch will be inferred.

EC3057D MTDS - Winter 2020

16

Synthesis of Combinational Logic – Functions

Example:

```
module or_nand_4 (enable, x1, x2, x3, x4, y);
  input enable, x1, x2, x3, x4;
  output y;
  assign y = or_nand(enable, x1, x2, x3, x4);

  function or_nand;
    input enable, x1, x2, x3, x4;
    begin
      or_nand = ~(enable & (x1 | x2) & (x3 | x4));
    end
  endfunction
endmodule
```

EC3057D MTDS - Winter 2020

17

Synthesis of Combinational Logic – Tasks

Example:

```
module or_nand_5 (enable, x1, x2, x3, x4, y);
  input enable, x1, x2, x3, x4;
  output y;
  reg y;
  always @ (enable or x1 or x2 or x3 or x4)
    or_nand (enable, x1, x2, x3, x4);

  task or_nand;
    input enable, x1, x2, x3, x4;
    output y;
    begin
      y = ~(enable & (x1 | x2) & (x3 | x4));
    end
  endtask
endmodule
```

EC3057D MTDS - Winter 2020

18

Construct to Avoid for Combinational Synthesis

- Edge-dependent event control
- Multiple event controls within the same behavior
- Named events
- Feedback loops
- Procedural-continuous assignment containing event or delay control
- **fork ... join** blocks
- **wait** statements
- External **disable** statements
- Procedural loops with timing
- Data dependent loops
- Tasks with timing controls
- Sequential UDPs


EC3057D MTDS - Winter 2020

19

Synthesis of Multiplexors

• Conditional Operator
 
```
module mux_4bits(y, a, b, c, d, sel);
  input [3:0] a, b, c, d;
  input [1:0] sel;
  output [3:0] y;
  assign y =
    (sel == 0) ? a :
    (sel == 1) ? b :
    (sel == 2) ? c :
    (sel == 3) ? d : 4'b0;
endmodule
```




EC3057D MTDS - Winter 2020

20

Synthesis of Multiplexors (cont.)

• CASE Statement
 
```
module mux_4bits (y, a, b, c, d, sel);
  input [3:0] a, b, c, d;
  input [1:0] sel;
  output [3:0] y;
  reg [3:0] y;
  always @ (a or b or c or d or sel)
    case (sel)
      0: y = a;
      1: y = b;
      2: y = c;
      3: y = d;
      default: y = 4'b0;
    endcase
endmodule
```




EC3057D MTDS - Winter 2020

21

Synthesis of Multiplexors (cont.)

• if .. else Statement
 
```
module mux_4bits (y, a, b, c, d, sel);
  input [3:0] a, b, c, d;
  input [1:0] sel;
  output [3:0] y;
  reg [3:0] y;
  always @ (a or b or c or d or sel)
    if (sel == 0) y = a; else
    if (sel == 1) y = b; else
    if (sel == 2) y = c; else
    if (sel == 3) y = d;
    else y = 4'b0;
endmodule
```



Note: CASE statement and if/else statements are more preferred and recommended styles for inferring MUX


EC3057D MTDS - Winter 2020

22

Unwanted Latches

- Unintentional latches generally result from incomplete case statement or conditional branch
- Example: case statement
 
```
always @ (sel_a or sel_b or data_a or data_b)
  case ({sel_a, sel_b})
    2'b10: y_out = data_a;
    2'b01: y_out = data_b;
  endcase
```



The latch is enabled by the "event or" of the cases under which assignment is explicitly made. e.g. ({sel_a, sel_b} == 2'b10) or ({sel_a, sel_b} == 2'b01)


EC3057D MTDS - Winter 2020

23

Unwanted Latches (cont.)

 - Example: if .. else statement

```
always @ (sel_a or sel_b or data_a or data_b)
  if ({sel_a, sel_b} == 2'b10)
    y_out = data_a;
  else if ({sel_a, sel_b} == 2'b01)
    y_out = data_b;
```



EC3057D MTDS - Winter 2020

24

Priority Logic


- When the branching of a conditional (if) is not mutually exclusive, or when the branches of a case statement are not mutually exclusive, the synthesis tool will create a priority structure.

Example:

```

module mux_4pri (y, a, b, c, d, sel_a, sel_b, sel_c);
input a, b, c, d, sel_a, sel_b, sel_c;
output y;
reg y;
always @ (sel_a or sel_b or sel_c or a or b or c or d)
begin
if (sel_a == 1) y = a; else
if (sel_b == 0) y = b; else
if (sel_c == 1) y = c; else
y = d;
end
endmodule

```

 

EC3057D MTDS - Winter 2020

25


VERILOG: Synthesis - Sequential Logic

- General Rule: A variable will be synthesized as a flip-flop when its value is assigned synchronously with an edge of a signal.
- Example:

```

module D_reg4a (Data_in, clock, reset, Data_out);
input [3:0] Data_in;
input clock, reset;
output [3:0] Data_out;
reg [3:0] Data_out;
always @ (posedge reset or posedge clock)
if (reset == 1'b1) Data_out <= 4'b0;
else Data_out <= Data_in;
endmodule

```

 

EC3057D MTDS - Winter 2020

26

Registered Combinational Logic


- Combinational logic that is included in a synchronous behavior will be synthesized with registered output.

Example:

```

module mux_reg (a, b, c, d, y, select, clock);
input [7:0] a, b, c, d;
output [7:0] y;
input [1:0] select;
reg [7:0] y;
always @ (posedge clock)
case (select)
0: y <= a; // non-blocking
1: y <= b; // same result with =
2: y <= c;
3: y <= d;
default: y <= 8'bx;
endcase
endmodule

```

 

EC3057D MTDS - Winter 2020

27


Verilog Shift Register

- Shift register can be implemented knowing how the flip-flops are connected

```

always @ (posedge clock) begin
if (reset == 1'b1) begin
reg_a <= 1'b0;
reg_b <= 1'b0;
reg_c <= 1'b0;
reg_d <= 1'b0;
end
else begin
reg_a <= Shift_in;
reg_b <= reg_a;
reg_c <= reg_b;
reg_d <= reg_c;
end
end

```

 

EC3057D MTDS - Winter 2020

28


Verilog Shift Register

- Shift register can be implemented using concatenation operation referencing the register outputs

```

module Shift_reg4 (Data_out, Data_in, clock, reset);
input Data_in, clock, reset;
output Data_out;
reg [3:0] Data_reg;
assign Data_out = Data_reg[0];
always @ (negedge reset or posedge clock) begin
if (reset == 1'b0) Data_reg <= 4'b0;
else Data_reg <= {Data_in, Data_reg[3:1]};
end
endmodule


```

 

EC3057D MTDS - Winter 2020

29

Verilog Ripple Counter

 

4-bit Ripple Counter

EC3057D MTDS - Winter 2020

30

Verilog Ripple Counter

```
module ripple_counter (clock, toggle, reset, count);
input clock, toggle, reset;
output [3:0] count;
reg [3:0] count;
wire c0, c1, c2;
assign c0 = count[0], c1 = count[1], c2 = count[2];


always @(posedge reset or posedge clock)
if (reset == 1'b1) count[0] <= 1'b0;
else if (toggle == 1'b1) count[0] <= ~count[0];

always @(posedge reset or negedge c0)
if (reset == 1'b1) count[1] <= 1'b0;
else if (toggle == 1'b1) count[1] <= ~count[1];

always @(posedge reset or negedge c1)
if (reset == 1'b1) count[2] <= 1'b0;
else if (toggle == 1'b1) count[2] <= ~count[2];

always @(posedge reset or negedge c2)
if (reset == 1'b1) count[3] <= 1'b0;
else if (toggle == 1'b1) count[3] <= ~count[3];
endmodule
```

Synthesis Result

 

EC3057D MTDS - Winter 2020


31

Sequential Logic

 - Example: D flip-flop with synchronous set/reset:

```
module dff(q, d, clk, set, rst);
input d, clk, set, rst;
output q;
reg q;
always @(posedge clk)
if (reset)
q <= 0;
else if (set)
q <= 1;
else
q <= d;
endmodule
```

We prefer *synchronous* set/reset,
but how would you specify
asynchronous preset/clear?



EC3057D MTDS - Winter 2020

32

Finite State Machines

```
module FSM1 (clk, rst, enable, data_in, data_out);
input clk, rst, enable;
input data_in;
output data_out;

/* Defined state encoding;
this style preferred over `defines */
parameter default=2'bxx;
parameter idle=2'b00;
parameter read=2'b01;
parameter write=2'b10;
reg data_out;
reg [1:0] state, next_state;

/* always block for sequential logic */
always @(posedge clk)
if (rst) state <= idle;
else state <= next_state;
```

- Style guidelines (some of these are to get the right result, and some just for readability)
 - Must have reset
 - Use separate always blocks for sequential and combination logic parts
 - Represent states with defined labels or enumerated types

EC3057D MTDS - Winter 2020

33

FSMs (cont.)

```
/* always block for CL */
always @(state or enable or data_in)
begin
case (state)
/* For each state def output and next */
idle : begin
data_out = 1'b0;
if (enable)
next_state = read;
else next_state = idle;
end
read : begin ... end
write : begin ... end

default : begin
next_state = default;
data_out = 1'bx;
end
endcase
end
endmodule
```

- Use CASE statement in an always to implement next state and output logic
- Always use default case and assert the state variable and output to 'bx':
 - Avoids implied latches
 - Allows use of don't cares leading to simplified logic
- "FSM compiler" within synthesis tool can re-encode your states; Process is controlled by using a synthesis attribute (passed in a comment).
 - Details in Synplify guide

EC3057D MTDS - Winter 2020

34


Bottom-line

- Have the hardware design clear in your mind when you write the verilog
- Write the verilog to describe that HW
- If you are very clear, the synthesis tools are likely to figure it out

EC3057D MTDS - Winter 2020

35

Reference

 

EC3057D MTDS - Winter 2020

36